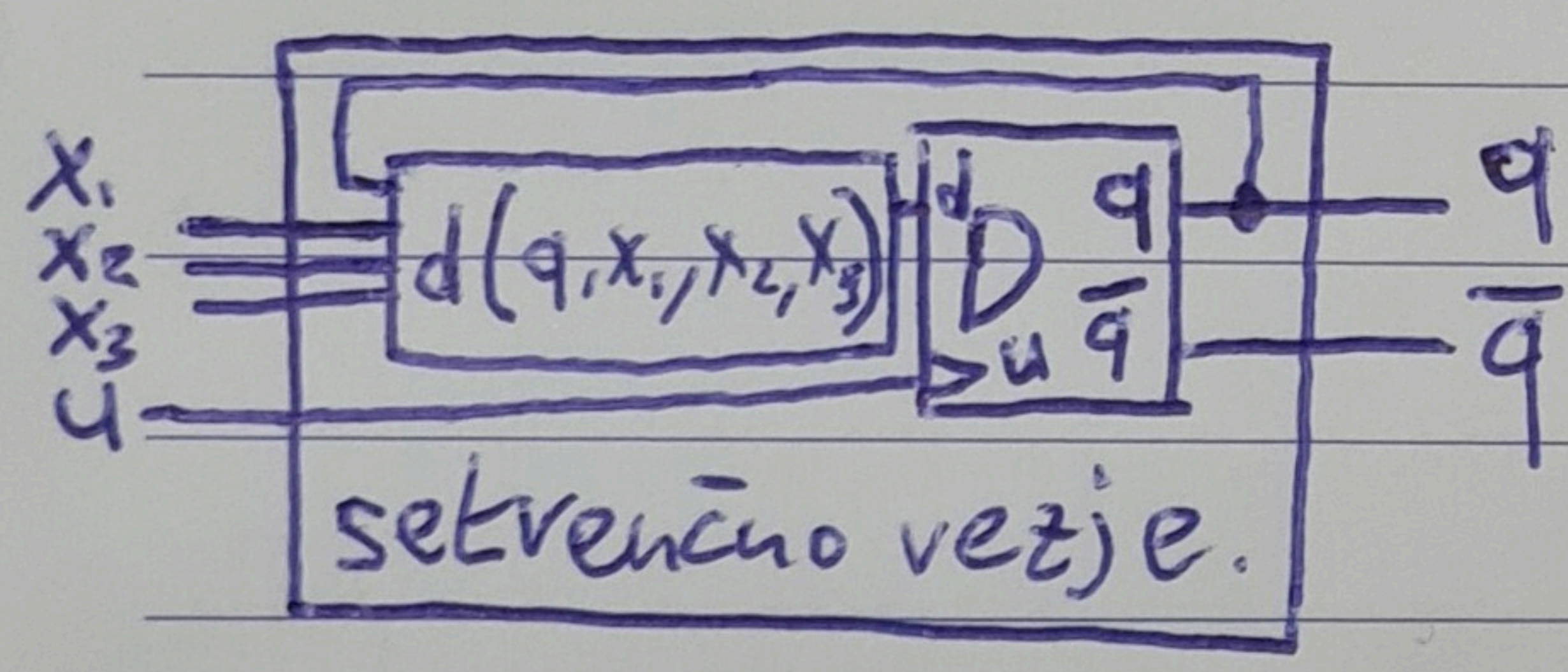



ODVDNO 8 FR 12 023 - 12-24 ŠIJANEC


q	x ₁	x ₂	x ₃	\bar{q}	f _{33} ^{...}	D ¹ q	m
0	0	0	0	1	0	1	0	0	0
0	0	0	1	1	0	1	0	0	1
0	0	1	0	1	0	1	0	0	2
0	0	1	1	1	1	1	0	1	3
0	1	0	0	1	0	1	0	0	4
0	1	0	1	1	1	1	0	1	5
0	1	1	0	1	1	0	0	0	6
0	1	1	1	1	0	1	0	0	7
1	0	0	0	0	0	1	0	0	8
1	0	0	1	0	0	1	0	0	9
1	0	1	0	0	0	1	0	0	10
1	0	1	1	0	0	1	1	1	11
1	1	0	0	0	0	1	0	0	12
1	1	0	1	0	0	1	0	0	13
1	1	1	0	0	0	1	0	0	14
1	1	1	1	0	1	1	0	1	15

$d(q, x_1, x_2, x_3) =$
 $= v(3, 5, 15)$
 $11)$




 $d(q, x_1, x_2, x_3) =$
 $\bar{q} \bar{x}_1 x_2 x_3 \vee \bar{q} x_1 \bar{x}_2 x_3 \vee$
 $\vee q x_1 x_2 x_3 \vee q \bar{x}_1 x_2 x_3$
 $= x_3 (\bar{q} (\bar{x}_1 x_2 \vee \bar{q} x_1 \bar{x}_2 \vee q x_1 x_2) \vee q (\bar{x}_1 x_2))$



 

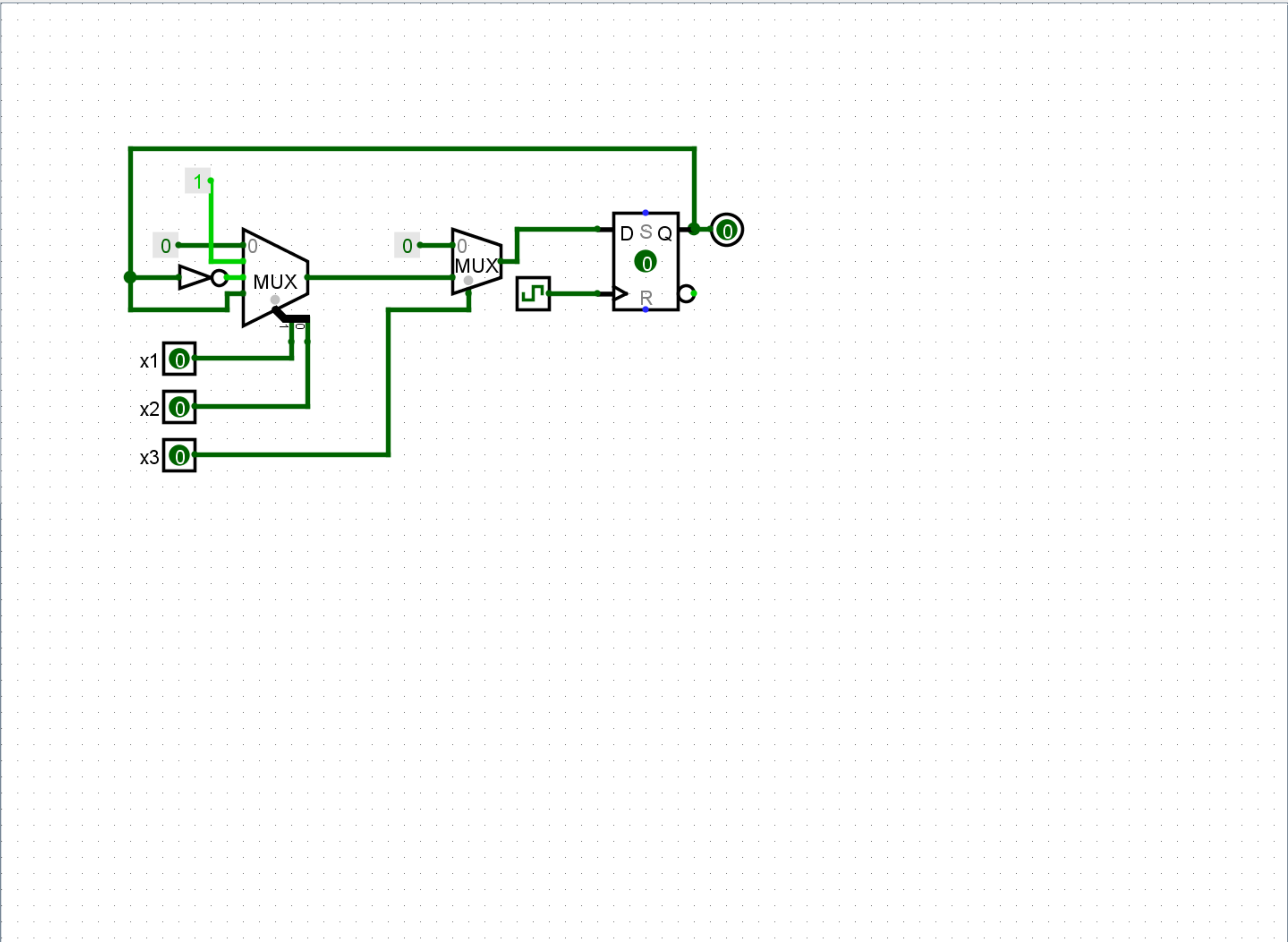- domaca_naloga_8
 - main
 - Wiring
 - Gates
 - Plexers
 - Arithmetic
 - Memory
 - Input/Output
 - HDL-IP
 - TCL
 - Base



Circuit: main	
Circuit Name	main
Shared Label	
Shared Label Facing	East
Shared Label Font	SansSerif Plain 12
Reference to VHDL architecture?	No
VHDL architecture file path	